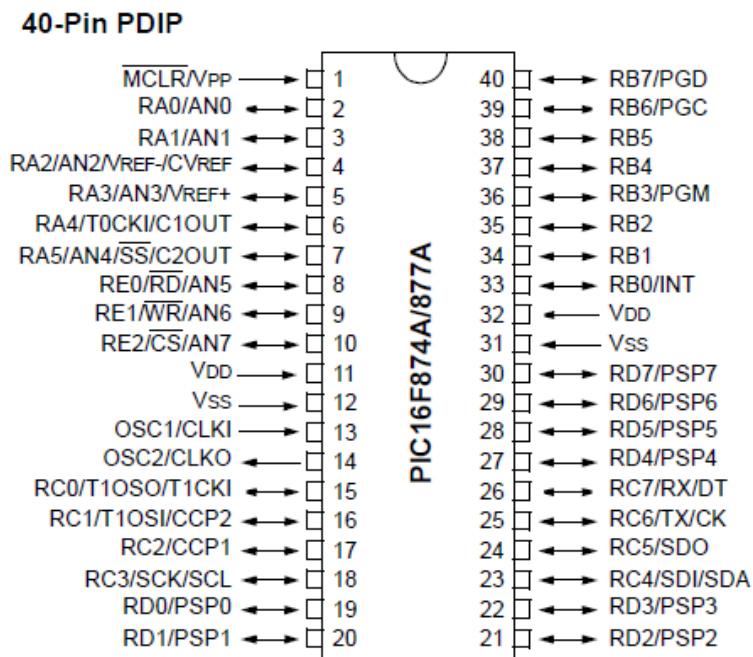


PIC Specifications



- 8000 line code
- 100000 write/erase
- 368 variable
- 40 years data storage in E²PROM
- 3 Timer/Counter. One of them is 16 bit, others 8 bit
- 10 bit ADC, 8 channel
- Codes are PIC compatible

Current Limits


- Max 25mA Output For one pin
- Max 150mA for total output

Oscillator Types

1- RC Oscillator

This type of oscillator is constructed with a resistor and a capacitor. You need to use specified values to acquire the desired frequency.

R	C	F _{osc}
10KΩ	20pF	625 KHz
10KΩ	220pF	80 KHz
10KΩ	0.1μF	80 KHz

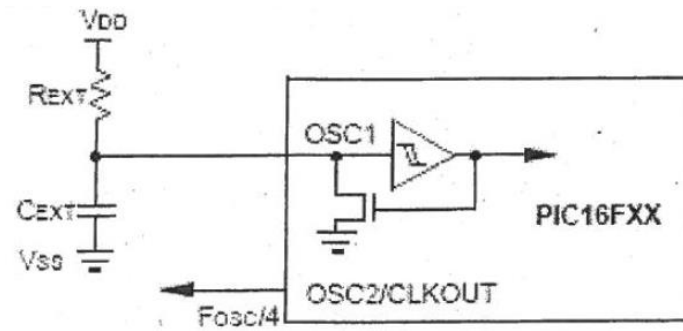


RC Oscillator Circuit

2- XT Oscillator

This type of oscillator is constructed with a crystal and twin capacitors. You need to use specified values to acquire the desired frequency.

C_1	C_2	XT (F_{osc})
100-150pF	100-150pF	100 KHz
15-33pF	15-33pF	2 MHz
15-33pF	15-33pF	4 MHz

*XT: Crystal Oscillator

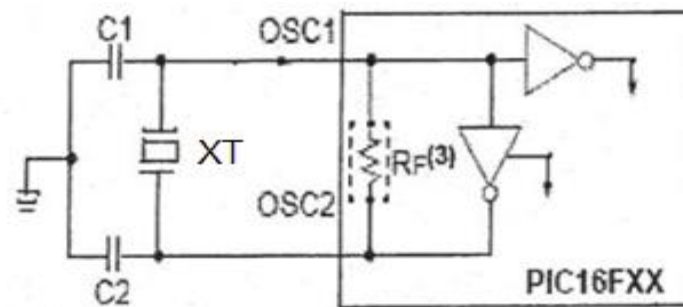


XT Oscillator Circuit

3- HS Oscillator

This type of oscillator is constructed with a crystal and twin capacitors. You need to use specified values to acquire the desired frequency. It is preferred for high speed operations.

C_1	C_2	XT (F_{osc})
15-33pF	15-33pF	4 MHz
15-33pF	15-33pF	20 MHz

*XT: Crystal Oscillator

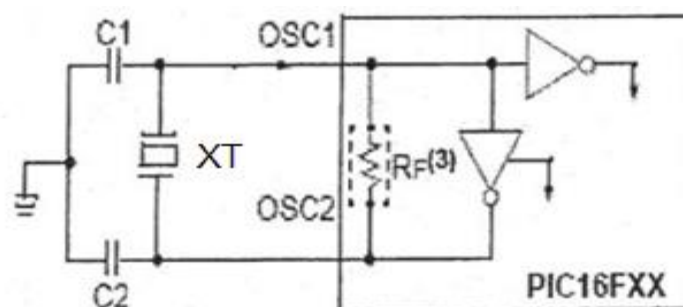


HS Oscillator Circuit

4- LP Oscillator

This type of oscillator is constructed with a crystal and twin capacitors. You need to use specified values to acquire the desired frequency. It is preferred for low power operations.

C ₁	C ₂	XT (F _{osc})
68-100pF	68-100pF	32 KHz
15-33pF	15-33pF	200 KHz

*XT: Crystal Oscillator

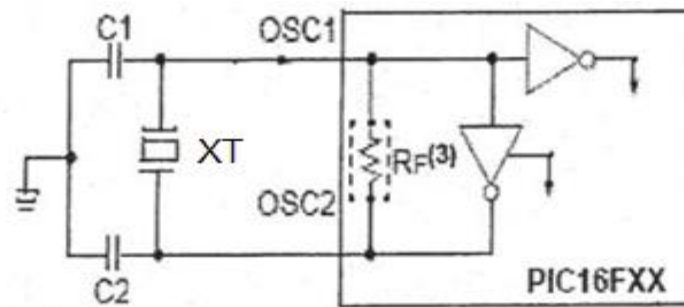

LP Oscillator Circuit

Cycle Time of An Instruction

For a 20MHz crystal

$$\frac{20}{4} = 5\text{MHz} \quad \frac{1}{5 \cdot 10^6} = 0.2\mu\text{s}$$

Reset Circuit of PIC

